

To scale transformer max voltage increase R1 and R2.
EXAMPLES
36V ac : R1=150ohm 3W, R42=82ohm 2W

To scale the current add 1 power transistor and 2 resistors every 2A.
Furthermore, the values of R12 and R23 must be proportionally decreased
as well as appropriately modifying the firmware.
EXAMPLES
5 final transistor (10A) R23=15k and R24=1500
2 final transistor (3A) R23=22k and R24=2700

